

1- Implement the Boolean function below using transistor-level Verilog coding.


$$f(A, B, C, D) = A'C + AB'C + BD' + A'C'D'$$

In your testbench, test the module for all different combinations of inputs.

For the first question, we simplify our function using Karnaugh map, then we use transistors, $\sim f$ and dual of $\sim f$ to create f .

$$\textcircled{1} f = A'C + AB'C + BD' + A'C'D'$$

K-Map \Rightarrow

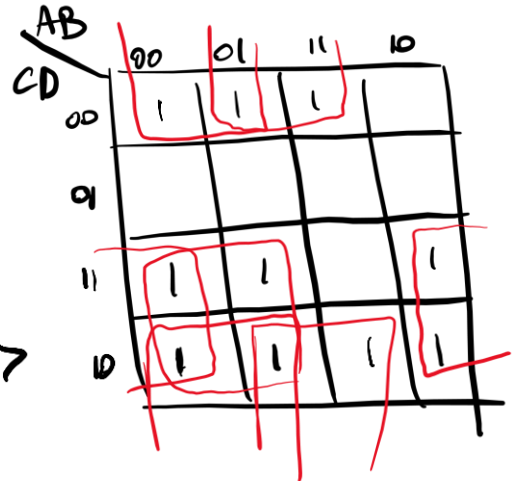



$$\bar{f} = A'D' + B'D' + A'C + B'C$$

$$\downarrow \bar{f}'$$

$$\bar{f} = (A+D) \cdot (B'+D) \cdot (A+C') \cdot (B+C')$$
 
$$D(\bar{f}') = (AD) + (B'D) + (AC') + (B'C')$$



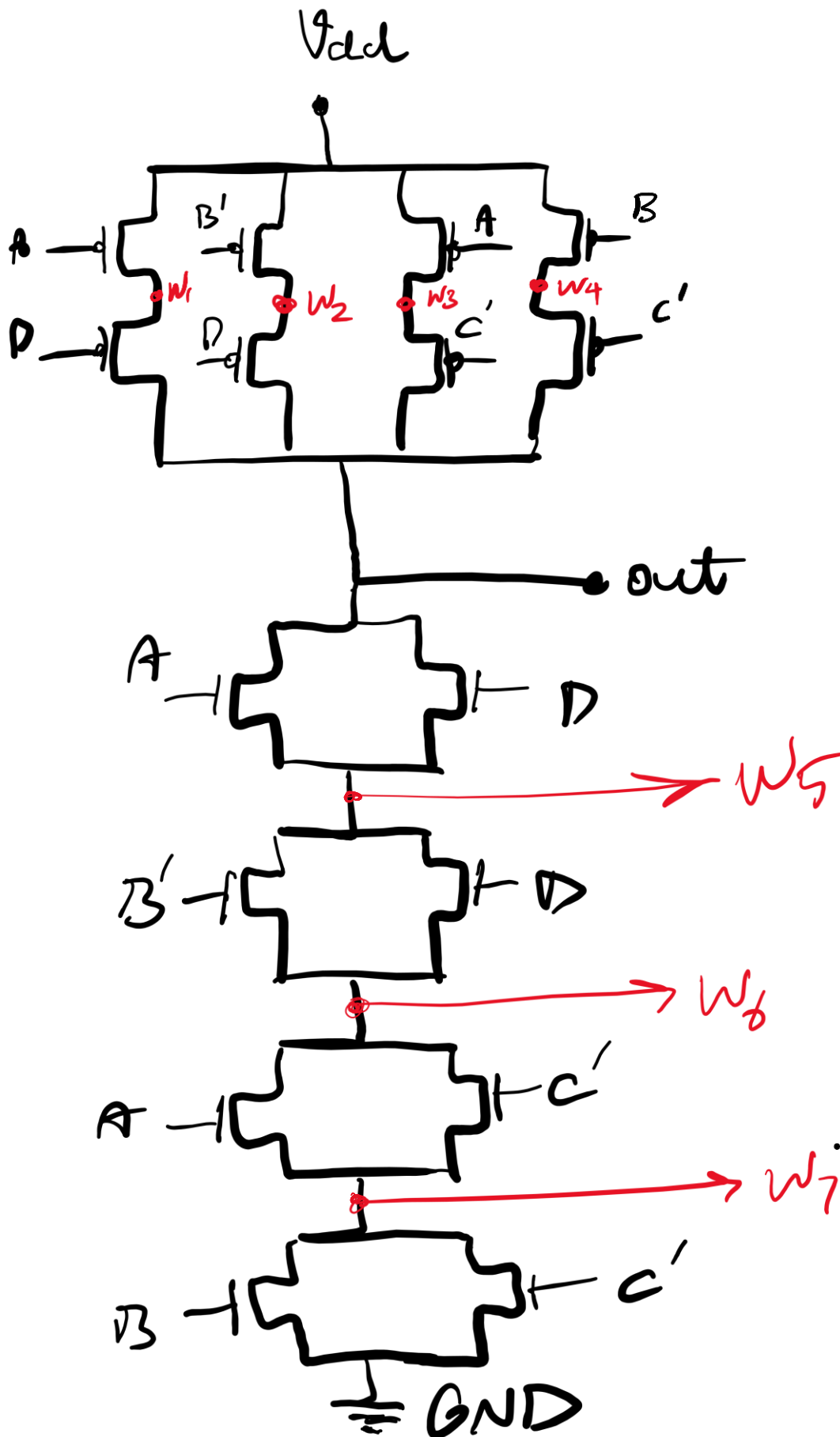

The Verilog code, implementation of module:

```

problem1 > V Foroutan.Nazanin.402243084.problem1.module.v
1  module fun(input a, a_not, b, b_not, c, c_not, d, d_not, output out);
2
3      wire w1, w2, w3, w4, w5, w6, w7;
4      supply1 vdd;
5      supply0 gnd;
6
7      pmos(w1, vdd, a);
8      pmos(out, w1, d);
9      pmos(w2, vdd, b_not);
10     pmos(out, w2, d);
11     pmos(w3, vdd, a);
12     pmos(out, w3, c_not);
13     pmos(w4, vdd, b);
14     pmos(out, w4, c_not);
15
16     nmos(out, w5, a);
17     nmos(out, w5, d);
18     nmos(w5, w6, b_not);
19     nmos(w5, w6, d);
20     nmos(w6, w7, a);
21     nmos(w6, w7, c_not);
22     nmos(w7, gnd, b);
23     nmos(w7, gnd, c_not);
24
25 endmodule

```

Part of test bench bench implementation:

```


problem1 > V Foroutan.Nazanin.402243084.problem1.testbench.v
1  `include "Foroutan.Nazanin.402243084.problem1.module.v"
2
3  module problem1_TestBench();
4
5      reg a, not_a, b, not_b, c, not_c, d, not_d;
6      wire out;
7      fun fun1(a, not_a, b, not_b, c, not_c, d, not_d, out);
8
9      initial begin
10
11         $dumpfile("waveform_problem1.vcd");
12         $dumpvars(0, problem1_TestBench);
13
14         #1;
15         a = 0;|
16         b = 0;
17         c = 0;
18         d = 0;
19         not_a = ~a;
20         not_b = ~b;
21         not_d = ~d;
22         not_c = ~c;
23         $display("A:%d , B:%d , C:%d , D:%d --> %d",a,b,c,d, out);
24

```

Picture of the outputs in the terminal:





```
[Running] Foroutan.Nazanin.402243084.problem1.testbench.v
VCD info: dumpfile waveform_problem1.vcd opened for output.
A:0 , B:0 , C:0 , D:0 --> 1
A:0 , B:0 , C:0 , D:1 --> 0
A:0 , B:0 , C:1 , D:0 --> 1
A:0 , B:0 , C:1 , D:1 --> 1
A:0 , B:1 , C:0 , D:0 --> 1
A:0 , B:1 , C:0 , D:1 --> 0
A:0 , B:1 , C:1 , D:0 --> 1
A:0 , B:1 , C:1 , D:1 --> 1
A:1 , B:0 , C:0 , D:0 --> 0
A:1 , B:0 , C:0 , D:1 --> 0
A:1 , B:0 , C:1 , D:0 --> 1
A:1 , B:0 , C:1 , D:1 --> 1
A:1 , B:1 , C:0 , D:0 --> 1
A:1 , B:1 , C:0 , D:1 --> 0
A:1 , B:1 , C:1 , D:0 --> 1
A:1 , B:1 , C:1 , D:1 --> 0
[Done] exit with code=0 in 0.024 seconds
```

The picture of the waves:

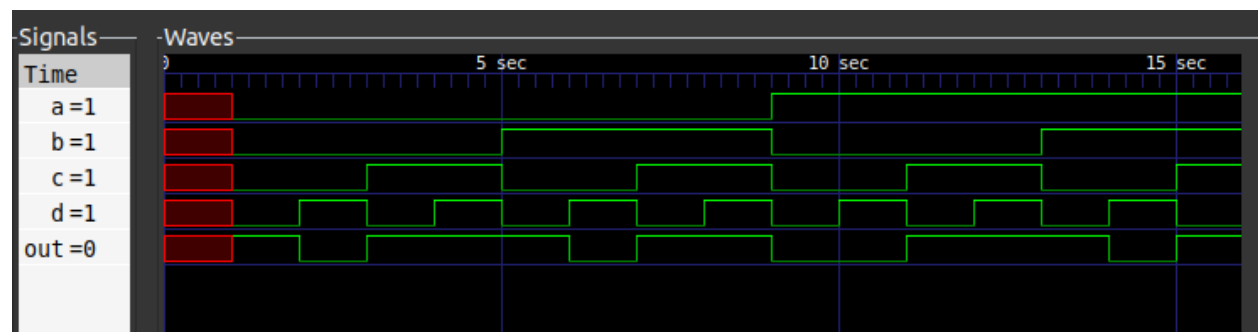

2- Implement an 4-bit signed adder using gate-level Verilog coding. The adder should have an overflow detector.

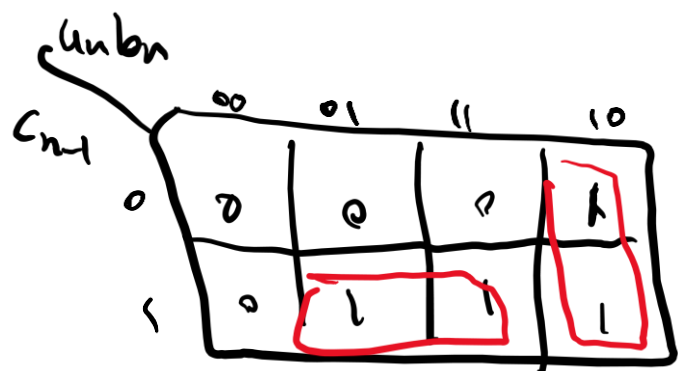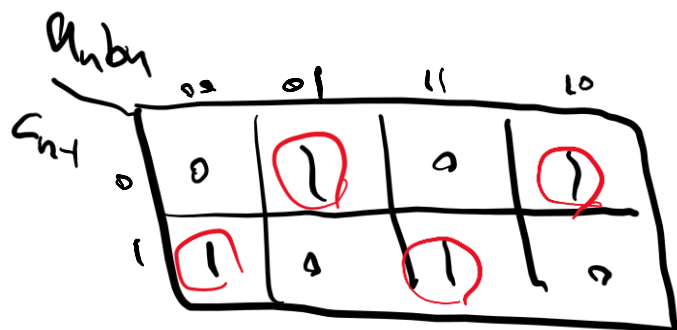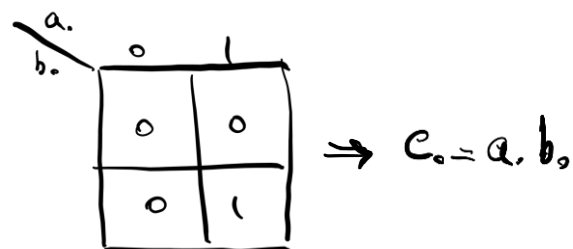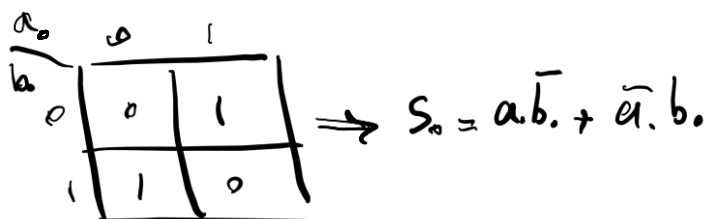In your testbench, test it for different inputs (once with two positive numbers without overflow, once with two positive numbers with overflow, once with two negative numbers without overflow, and once with two negative numbers with overflow).



a_{n-1}	a_n	b_{n-1}	b_n	S_n	C_n
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	0	1

$$S_n = \overline{a_n} (b_n \oplus C_{n-1}) + a_n (\overline{b_n} \oplus C_{n-1})$$

$$C_n = a_n b_n + b_n C_{n-1}$$

$a_3 b_3$

S_3

	00	01	11	10
0	0	0	1	0
1	1	0	0	0

overflow $\Rightarrow a_3 b_3 \overline{S_3} + \overline{a_3} \overline{b_3} S_3$

For the module implementation I built one full adder then I used cascade to build the four bit adder.

one bit adder:

```

problem2 > V Foroutan.Nazanin.402243084.problem2.module.v
1  module full_adder(input A, B, cin, output sum, cout);
2      wire AandB, AandCin, BandCin, AxorB;
3
4      xor(AxorB, A, B);
5      xor(sum, AxorB, cin);
6
7      and(AandB, A, B);
8      and(AandCin, A, cin);
9      and(BandCin, B, cin);
10     or(cout, AandB, AandCin, BandCin);
11
12 endmodule
13

```

Four bit adder:

```

14
15 module four_bit_adder(input [3:0] A, B, output [3:0] sum, output overflow, cout);
16     wire c1, c2, c3; // Declare cout wire
17     wire A3andB3andS3not, A3notandB3notandS3;
18
19     full_adder fa1(A[0], B[0], 1'b0, sum[0], c1);
20     full_adder fa2(A[1], B[1], c1, sum[1], c2);
21     full_adder fa3(A[2], B[2], c2, sum[2], c3);
22     full_adder fa4(A[3], B[3], c3, sum[3], cout);
23
24     // overflow detection
25     and(A3andB3andS3not, A[3], B[3], ~sum[3]);
26     and(A3notandB3notandS3, ~A[3], ~B[3], sum[3]);
27     or(overflow, A3andB3andS3not, A3notandB3notandS3);
28
29 endmodule

```

Part of test bench:

```

1  `include "Foroutan.Nazanin.402243084.problem2.module.v"
2
3  module problem2_testbench;
4      reg [3:0] A;
5      reg [3:0] B;
6      wire [3:0] Sum;
7      wire overflow;
8      wire cout;
9
10     // Instantiate the four_bit_adder module using positional port mapping
11     four_bit_adder adder(A, B, Sum, overflow, cout);
12
13     initial begin
14         $dumpfile("waveform_problem2.vcd");
15         $dumpvars(0, problem2_testbench);
16
17         // Test case 1: Two positive numbers without overflow
18         A = 4'b0010; // 2
19         B = 4'b0011; // 3
20         #10;
21         $display("A = %b, B = %b, Sum = %b, Overflow = %b, Cout = %b", A, B, Sum, overflow, cout);
22

```


The output shown in terminal:

```

[Running] Foroutan.Nazanin.402243084.problem2.testbench.v
VCD info: dumpfile waveform_problem2.vcd opened for output.
A = 0010, B = 0011, Sum = 0101, Overflow = 0, Cout = 0
A = 0111, B = 0101, Sum = 1100, Overflow = 1, Cout = 0
A = 1101, B = 1011, Sum = 1000, Overflow = 0, Cout = 1
A = 1001, B = 1001, Sum = 0010, Overflow = 1, Cout = 1
[Done] exit with code=0 in 0.024 seconds

```

The wave shown in gtk wave:

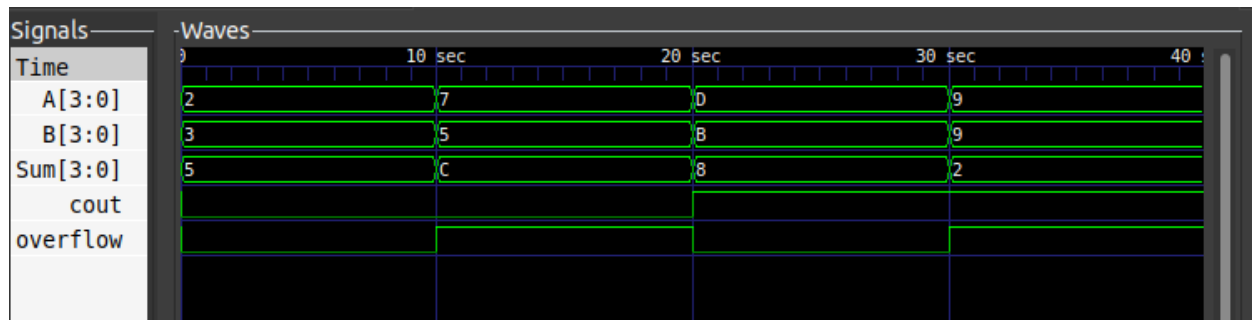

3- Implement an ALU with two 6 bit signed inputs A and B and with 4 different operation modes mentioned below.

0- $(A \lll 2) + (B \ggg 1)$

1- $A + 3B$

2- $-B$

3- $|2A - B|$

For the ALU implementation we were supposed to build modules for each operation and then use them to make the alu.

```

20
21 module shift(input [5:0] A, B, output [5:0] res, output cout);
22     wire [5:0] shifted_res;
23     assign shifted_res = (A <<< 2) + (B >>> 1);
24     assign res = shifted_res;
25     assign cout = (shifted_res[5] != res[5]); // Simple carry out
26 endmodule
27
28
29 module add(input [5:0] A, B, output [5:0] res, output cout);
30     assign {cout, res} = A + 3*B;
31 endmodule
32
33
34 module neg(input [5:0] B, output [5:0] res);
35     assign res = -B;
36 endmodule
37
38
39 module abs(input [5:0] A, B, output [5:0] res);
40     assign res = (2*A - B > 0 ? 2*A - B : -(2*A - B));
41 endmodule
42

```


The ALU using modules:

```

1  module ALU(
2      input [5:0] A, B,
3      input [1:0] op_code,
4      output [5:0] out,
5      output cout
6  );
7      wire [5:0] res0, res1, res2, res3;
8      wire cout_add, cout_shift;
9
10     shift zero(A, B, res0, cout_shift);
11     add one(A, B, res1, cout_add);
12     neg two(B, res2);
13     abs three(A, B, res3);
14
15     assign out = op_code[1] ? (op_code[0] ? res3 : res2) : (op_code[0] ? res1 :
16         res0);
17     assign cout = (op_code == 2'b01) ? cout_add : (op_code == 2'b00) ? cout_shift :
18         1'b0; // cout for add and shift operations
19
20 endmodule

```


Part of test bench:

```


1  `include "Foroutan.Nazanin.402243084.problem3.module.v"
2
3  module problem3_testbench();
4      reg[5:0] A, B;
5      reg[1:0] op;
6      wire[5:0] out;
7      wire cout;
8
9      ALU ALU_6bit (A, B, op, out, cout);
10
11     initial begin
12         $dumpfile("waveform_problem3.vcd");
13         $dumpvars(0, problem3_testbench);
14
15         A = -5;
16         B = 20;
17         op = 2'b00;
18         #1;
19         $display("A: %b\nB: %b\nOperation: %b\nOutput: %b\nCarry Out: %b\n", A, B,
20             op, out, cout);
21
22         A = 5;
23         B = 10;
24         op = 2'b01;
25         #1;
26         $display("A: %b\nB: %b\nOperation: %b\nOutput: %b\nCarry Out: %b\n", A, B,
27             op, out, cout);
28     end
29 endmodule

```

The waves:

 

 4- Design and implement a counter that only count odd numbers from 1 to 9.



* Reset = 0 → Returns to S₁

The module code:


```

1  module odd_counter (
2      input wire clk,
3      input wire reset, // Add reset input
4      output reg [3:0] count
5  );
6
7  always @(posedge clk or posedge reset) begin
8      if (reset) begin
9          count <= 4'b0001; // Reset to 1
10     end else begin
11         case (count)
12             4'b0001: count <= 4'b0011;
13             4'b0011: count <= 4'b0101;
14             4'b0101: count <= 4'b0111;
15             4'b0111: count <= 4'b1001;
16             4'b1001: count <= 4'b0001;
17             default: count <= 4'b0001; // Default to 1
18         endcase
19     end
20 end
21
22 endmodule
  
```

The test bench code:

```
3  module odd_counter_tb;
4
5  reg clk;
6  reg reset; // Add reset signal
7  wire [3:0] count;
8
9  // Instantiate the odd_counter module
10 odd_counter uut (
11     .clk(clk),
12     .reset(reset), // Connect reset signal
13     .count(count)
14 );
15
16 // Clock generation
17 initial begin
18     clk = 0;
19     forever #5 clk = ~clk; // Toggle clock every 5 time units
20 end
21
22 initial begin
23     $monitor("Time = %0t, Count = %0d", $time, count);
24
25     // Initial reset
26     reset = 1; // Apply reset
27     #10;
28     reset = 0; // Release reset
29
30     // Wait for count to be 5
31     wait (count == 4'b0101);
32     reset = 1;
33     #10;
34     reset = 0;
35
36     #100; // Run for additional 100 time units
37
38     $finish;
39 end
```

Waves and outputs:

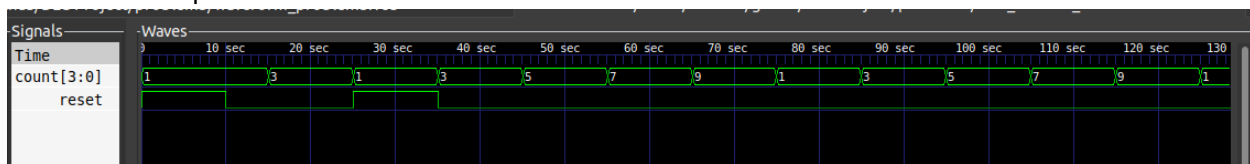

```

Time = 0, Count = 1
Time = 15, Count = 3
Time = 25, Count = 1
Time = 35, Count = 3
Time = 45, Count = 5
Time = 55, Count = 7
Time = 65, Count = 9
Time = 75, Count = 1
Time = 85, Count = 3
Time = 95, Count = 5
Time = 105, Count = 7
Time = 115, Count = 9
Time = 125, Count = 1
Time = 135, Count = 3
    
```

5- Design and implement a sequence detector to detect 0110110 sequence.

In the Verilog code the main part for state machine:

```

// next state logic
always @(*) begin
    if(reset == 1) begin
        next_state = S0;
    end else begin
        case (current_state)
            S0: next_state = (in_bit == 0) ? S1 : S0;
            S1: next_state = (in_bit == 1) ? S2 : S1;
            S2: next_state = (in_bit == 1) ? S3 : S1;
            S3: next_state = (in_bit == 0) ? S4 : S0;
            S4: next_state = (in_bit == 1) ? S5 : S1;
            S5: next_state = (in_bit == 1) ? S6 : S1;
            S6: next_state = (in_bit == 0) ? S7 : S0;
            S7: next_state = (in_bit == 0) ? S1 : S5;
            default: next_state = S0;
        endcase
    end
end
    
```


The encoding for the state machines:

```
// State encoding
parameter S0 = 3'b000;
parameter S1 = 3'b001;
parameter S2 = 3'b010;
parameter S3 = 3'b011;
parameter S4 = 3'b100;
parameter S5 = 3'b101;
parameter S6 = 3'b110;
parameter S7 = 3'b111;
```


The outputs shown in terminal:

```
[Running] Foroutan.Nazanin.402243084.problem5.testbench.v
Time: 5000 | reset: 1 | in_bit: 0 | Current State: 000 | Next State: 000 | seq_detected: 0
Time: 15000 | reset: 0 | in_bit: 0 | Current State: 000 | Next State: 001 | seq_detected: 0
Time: 25000 | reset: 0 | in_bit: 1 | Current State: 001 | Next State: 010 | seq_detected: 0
Time: 35000 | reset: 0 | in_bit: 1 | Current State: 010 | Next State: 011 | seq_detected: 0
Time: 45000 | reset: 0 | in_bit: 0 | Current State: 011 | Next State: 100 | seq_detected: 0
Time: 55000 | reset: 0 | in_bit: 1 | Current State: 100 | Next State: 101 | seq_detected: 0
Time: 65000 | reset: 0 | in_bit: 1 | Current State: 101 | Next State: 110 | seq_detected: 0
Time: 75000 | reset: 0 | in_bit: 0 | Current State: 110 | Next State: 111 | seq_detected: 0
Time: 85000 | reset: 0 | in_bit: 1 | Current State: 111 | Next State: 101 | seq_detected: 1
Time: 95000 | reset: 0 | in_bit: 0 | Current State: 101 | Next State: 001 | seq_detected: 0
[Done] exit with code=0 in 0.025 seconds
```

The diagram:

 

The solution for the state machine:

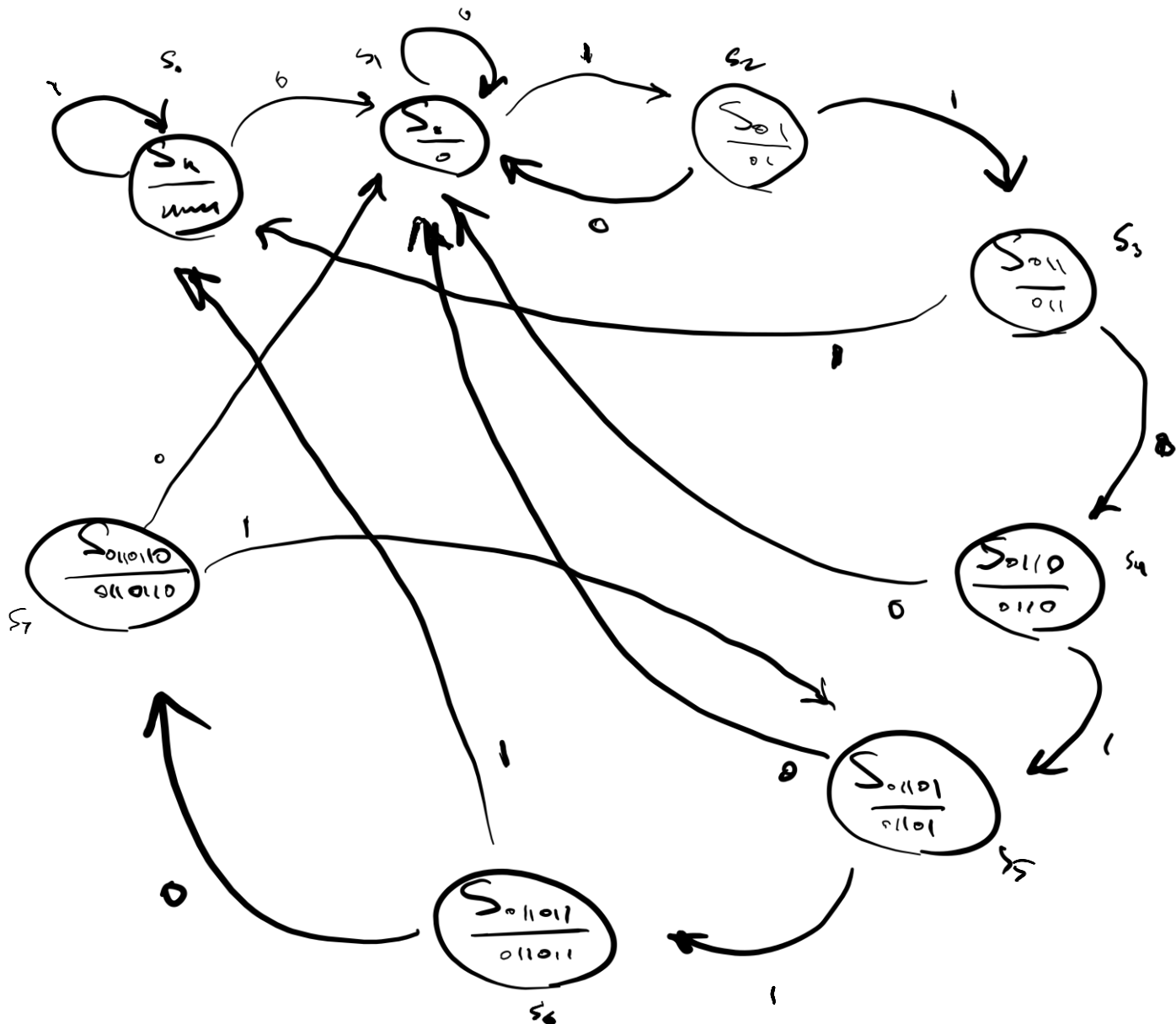

$$S_7 \rightarrow S_0$$

$$S_{0110} \rightarrow S_4$$

$$S_0 \rightarrow S_1$$

$$S_{01101} \rightarrow S_5$$

$$S_{01} \rightarrow S_2$$

$$S_{011011} \rightarrow S_6$$

$$S_{011} \rightarrow S_3$$

$$S_{0110110} \rightarrow S_7$$